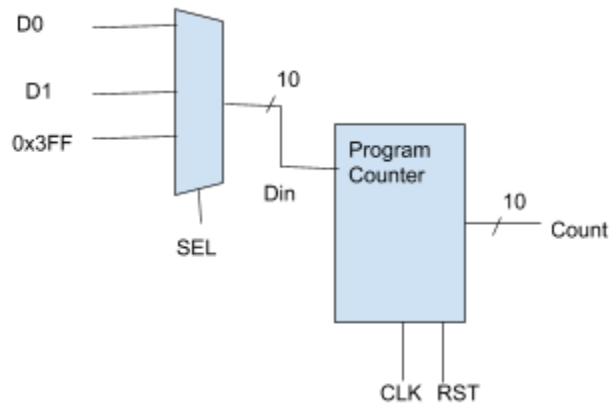



Black Box Diagram :




Behavior Design :

In this RAT assignment, we designed a program counter with a multiplex input. We coded this through modules in system verilog. The multiplexor decided on the input from either the stack, immediate input, or an interrupt.

Structure Design :

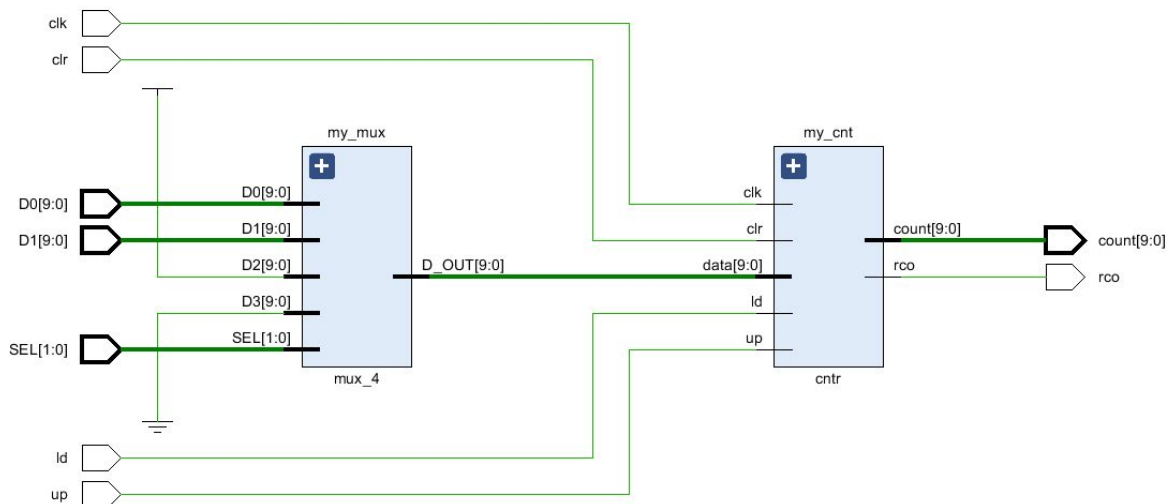

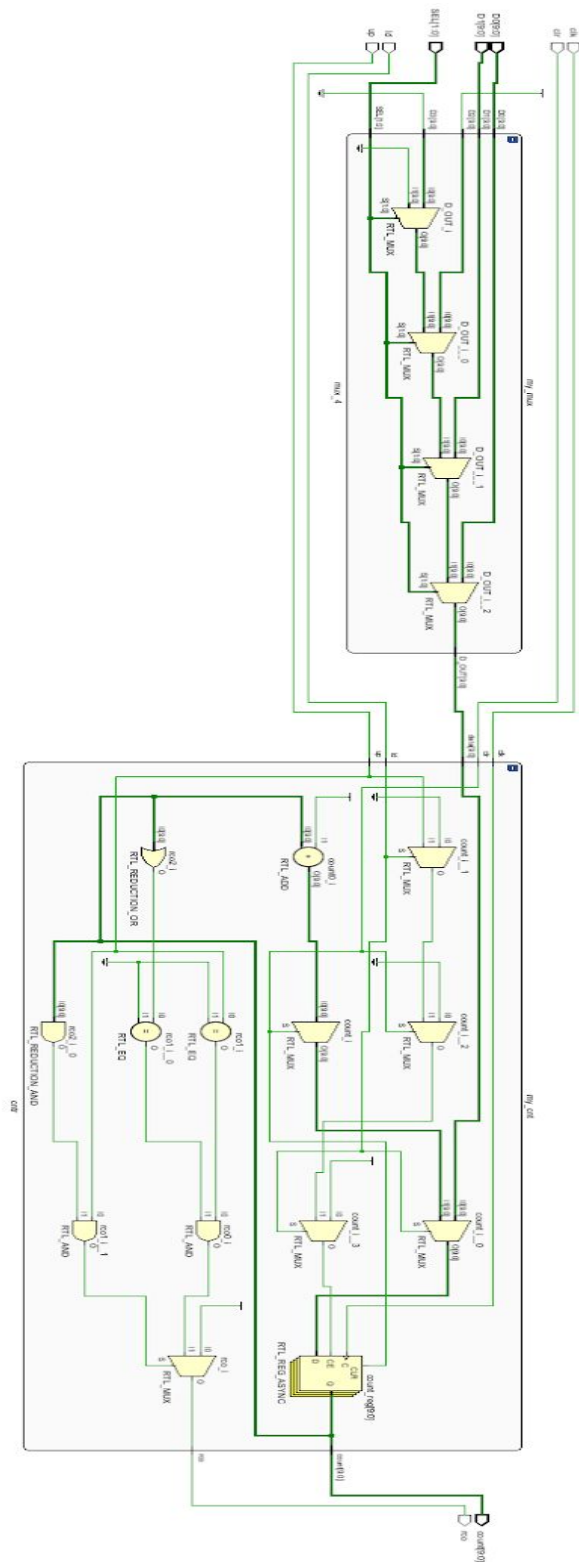


Verification :

Values:

Name	Value
CLK	0
> D0[9:0]	0ff
> D1[9:0]	0aa
> SEL[1:0]	2
clr	0
ld	0
up	1
rco	0
> count[9:0]	001

Test Bench Output

 

Values	Output
10ns-20ns SEL = 2'b01; D0 = 'hFF; D1 = 'hAA; clr = 1'b0; ld = 1'b1; up = 1'b1;	0xAA loaded into counter from D1
20ns-30ns SEL = 2'b01; D0 = 'hFF; D1 = 'hAA; clr = 1'b1; ld = 1'b1; up = 1'b1;	It can be seen in the Figure above that the counter is cleared.
30ns-110ns SEL = 2'b10; D0 = 'hFF; D1 = 'hAA; clr = 1'b0; ld = 1'b1; up = 1'b1;	Here the interrupt is being loaded and can be seen counting up from 1 due to the fact that 0x3FF is the max address.

The test cases shown above in the table were chosen to represent the individual inputs from the multiplexor. Through these test cases we could see that the functionality works. See the table above for more about each test case.

System Verilog Source Code :

```

module PC(D0, D1, clk, ld, up, SEL, clr, rco, count);

    input [9:0] D0, D1;
    input [1:0] SEL;
    input clk, clr, ld, up;

    output rco;
    output [9:0] count;

    wire [9:0] data;

    mux_4 my_mux(
        .SEL      (SEL),
        .D0       (D0),
        .D1       (D1),
        .D2       (10'b111111111),
        .D3       (10'b000000000),
        .D_OUT    (data)
    );

    cntr my_cnt(
        .clk      (clk),
        .clr      (clr),
        .up       (up),
        .ld       (ld),
        .data     (data),
        .count    (count),
        .rco      (rco)
    );

endmodule

module cntr(clk, clr, up, ld, data, count, rco);
    input  clk, clr, up, ld;
    input  [9:0] data;
    output reg [9:0] count;
    output reg rco;

```

```

always_ff @(posedge clr, posedge clk)
begin
    if (clr == 1'b1)          // asynch reset
        count <= 0;
    else if (ld == 1'b1)      // load new value
        count <= data;
    else if (up == 1'b1)      // count up (increment)
        //count <= count + 1'b1;
        count++;
end

// handles the RCO, which is direction dependent
always_ff @(count, up)
begin
    if ( up == 1 && count == 1'b1)
        rco = 1'b1;
    else if (up == 0 && count == 1'b0)
        rco = 1'b1;
    else
        rco = 1'b0;
end

endmodule

module mux_4(SEL, D0, D1, D2, D3, D_OUT);
    input  [1:0] SEL;
    input  [9:0] D0, D1, D2, D3;
    output reg [9:0] D_OUT;

    always @(SEL, D0, D1, D2, D3)
    begin
        if      (SEL == 0)  D_OUT = D0;
        else if (SEL == 1)  D_OUT = D1;
        else if (SEL == 2)  D_OUT = D2;
        else if (SEL == 3)  D_OUT = D3;
        else
            D_OUT = 0;
    end
end

endmodule

```